

# Lecture -9


## 555 Timer

Prepared By: Asif Mahfuz



 
# Introduction

- 555 timer IC was first introduced around 1971 by Signetics Corporation.
- It was called the “The IC Time Machine”.
- The IC 555 timer is used in different applications like an oscillator, pulse generation, timer.
- The name is derived from the three 5k resistors in the IC.
- The operating range of the IC ranges from 4.5V – 15V DC supply.
- The functional parts of the 555 timer IC include flip-flop, voltage divider and a comparator.
- The main function of this IC is to generate an accurate timing pulse.



 
# Pin Configuration

- **GND:** All voltages are measured with respect to this terminal.
- **TRIGGER:** The output of the timer depends on the amplitude of the external trigger pulse applied to this pin. When a negative going pulse of amplitude greater than  $\frac{1}{3} V_{CC}$  is applied to this pin, the output of the timer is high. The output remains high as long as the trigger terminal is held at low voltage.
- **OUTPUT:** The output of the timer is measured here with respect to ground.
- **RESET:** The 555 timer can be disabled/ reset by applying a negative pulse to this pin. When the reset function is not in use, the reset terminal should be connected to  $+V_{CC}$  to avoid any possibility of false triggering.



 
# Pin Configuration (contd...)

- **CONTROL VOLTAGE:** An external voltage applied to this terminal changes the threshold as well as the triggering voltage. Thus by imposing a voltage on this pin or by connecting a pot between this pin and ground, the pulse width of the output waveform can be varied. When not used, the control pin should be bypassed to ground with a  $0.01\mu\text{F}$  Capacitor to prevent any noise problem.
- **THRESHOLD:** When the voltage at this pin is greater than or equal to the threshold voltage,  $\frac{2}{3} V_{CC}$ , the output of the timer is low.
- **DISCHARGE:** The pin is connected internally to the collector of transistor Q. When the output is high Q is OFF and acts as an open circuit to external capacitor C connected across it. On the other hand, when the output is low, Q is saturated and acts as a short circuit, shorting out the capacitor C to ground.
- **+V<sub>CC</sub>:** The supply voltage of +5V to +18V is applied to this pin with respect to ground.



# Functional Block Diagram

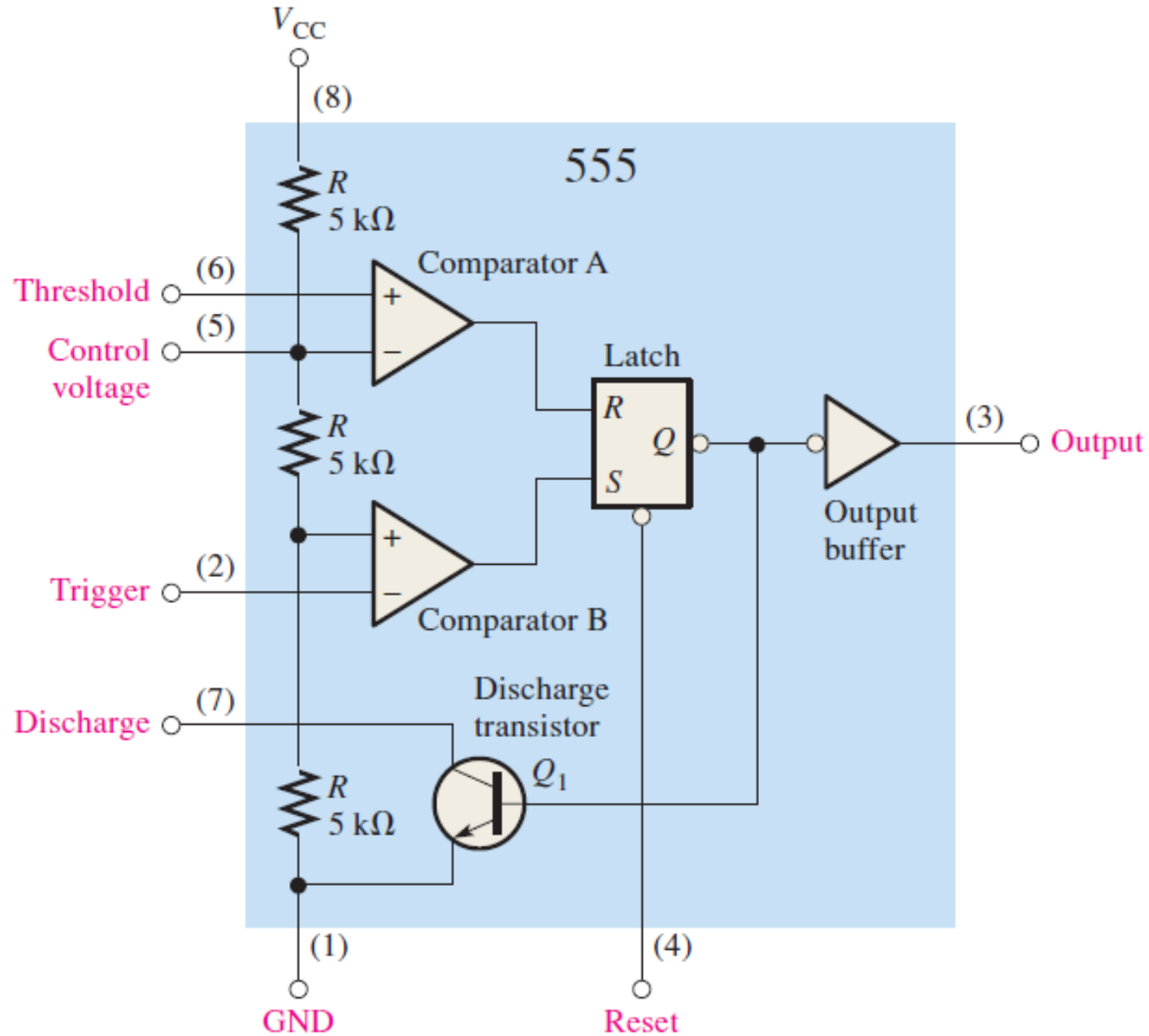


# Function of the Components

- **5K RESISTORS NETWORK:** The resistor network provide the two comparators with the reference voltage. Each resistor drops a voltage of  $\frac{1}{3} V_{CC}$ . So for the upper comparator the reference voltage is  $\frac{2}{3} V_{CC}$  and for the lower comparator the reference voltage is  $\frac{1}{3} V_{CC}$ .
- **VOLTAGE COMPARATORS:** The voltage comparator gives a positive output when the voltage in the +ve input is higher than the -ve input. And when the -ve input is higher than the positive input, the output is 0. When the output of the upper comparator is high, it resets the Flip-Flop and when the output of the lower comparator is high, it sets the Flip-Flop.
- **R-S FLIP-FLOP:** The R-S Flip-Flop is used as a memory element to hold the output.  $\bar{Q}$  is connected to the output pin and  $Q$  is connected to an NPN transistor.
- **NPN TRANSISTOR:** When a positive voltage is given to the NPN transistor, the NPN transistor goes to saturation. This shorts the emitter and collector terminals. Therefore the discharge pin gets shorted to the ground.
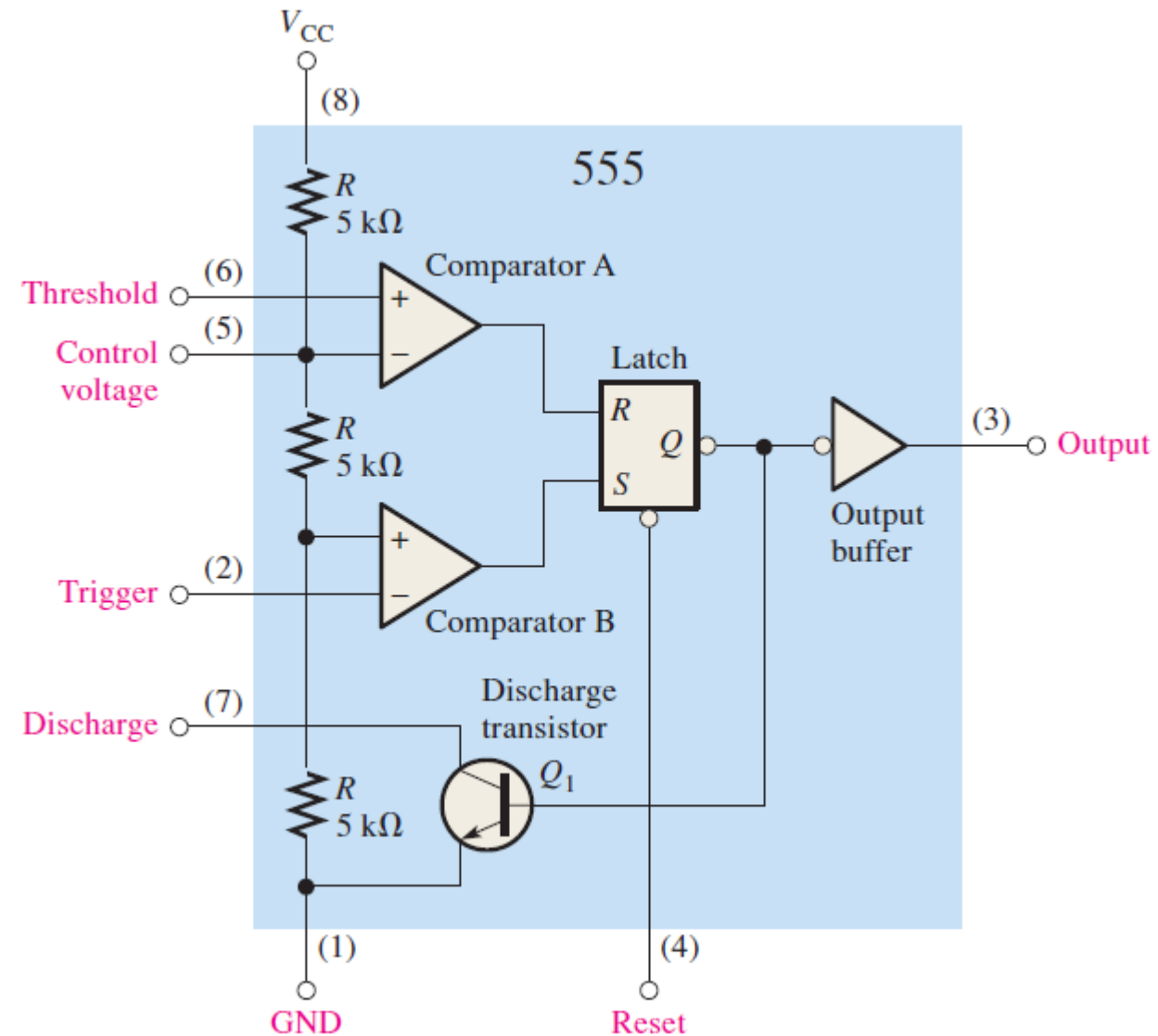
# Basic Operation

- When the normally HIGH trigger input momentarily goes below  $1/3 V_{CC}$ , the output of the comparator B switches from LOW to HIGH and sets the S-R latch ( $Q=1$ ) causing the output (pin 3) to go HIGH and thus also turning the discharge transistor Q1 OFF.
- When the LOW threshold input goes above  $2/3 V_{CC}$  and causes the output of comparator A to switch from LOW to HIGH. This resets the latch ( $Q=0$ ), causing the output (pin 3) to go back LOW and thus turning the discharge transistor ON.
- Note: The trigger and threshold inputs are controlled by external components to produce either monostable or astable operation.



# Modes of Operation

- **Astable Mode:** In this mode the output of a 555 timer switches between the two unstable states without any external trigger. The feature of the 555 timer can be used to generate continuous rectangular wave.
- **Monostable Mode (One-shot):** In this mode, the 555 timer has one stable state. Whenever, the trigger is made low, the 555 timer switches into the unstable state. Then after a certain time, determined by the external combination of resistor and capacitor, the 555 time returns to its stable state.
- **Bistable Mode:** In this mode, the 555 timer has two stable states. Each time when the 555 timer is triggered, the timer switches from one stable state to the other.




# Astable Mode

Astable Mode Schematic:


The components which determine the operation are:

- Two resistors ( $R_1$  and  $R_2$ )
- One capacitor ( $C_1$ )

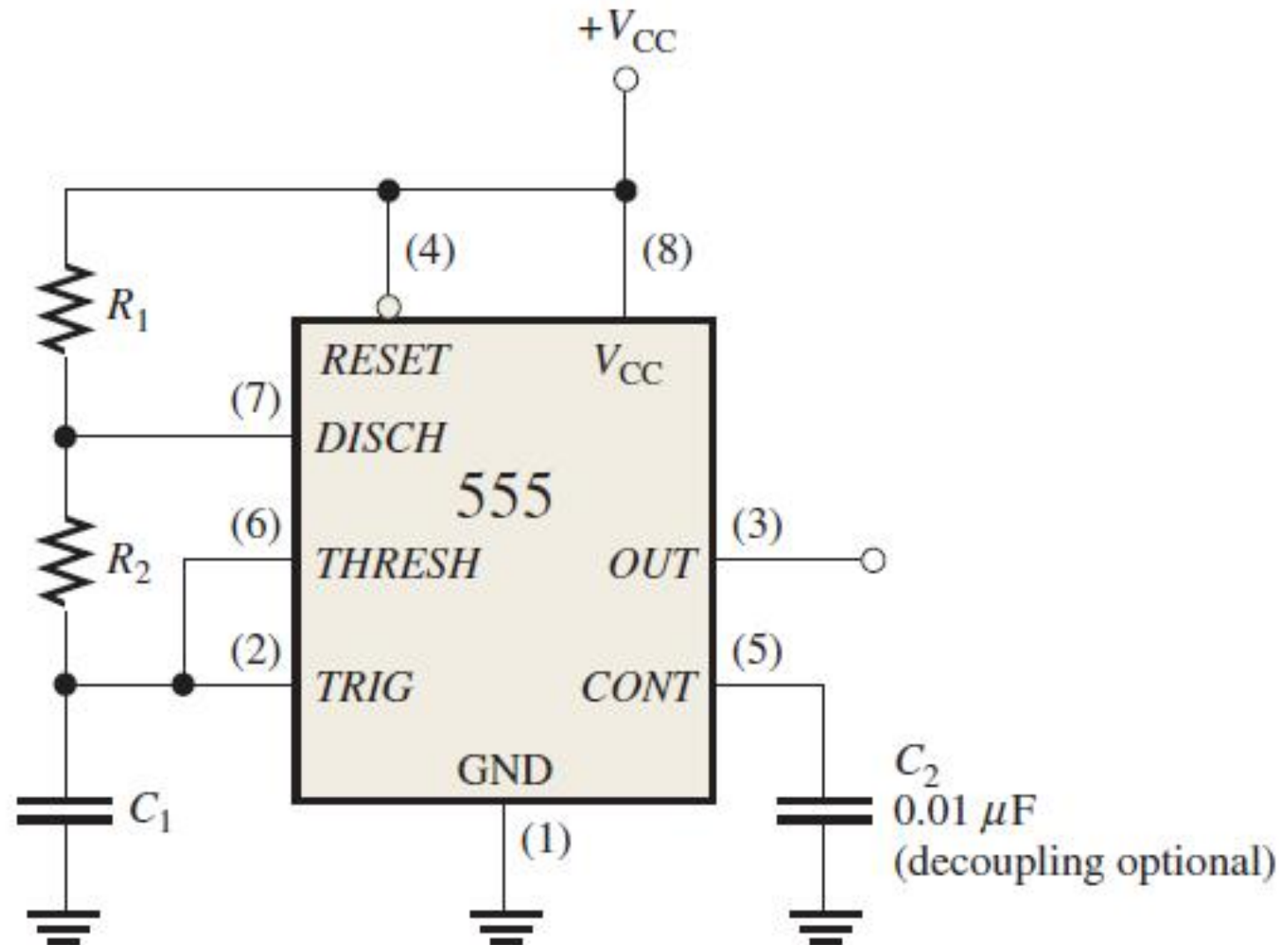The output of this circuit is a square wave pulse.




# Astable Mode

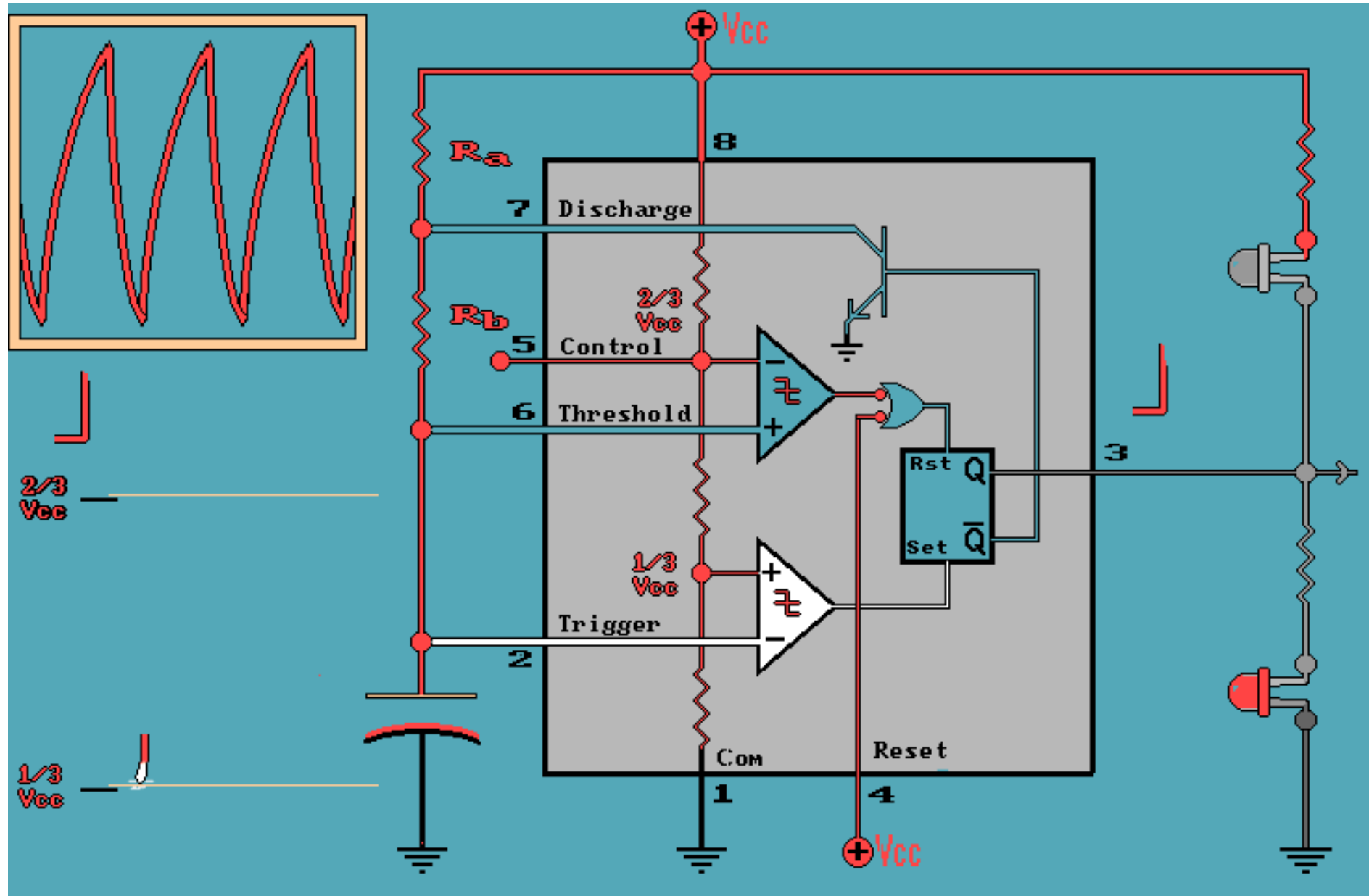

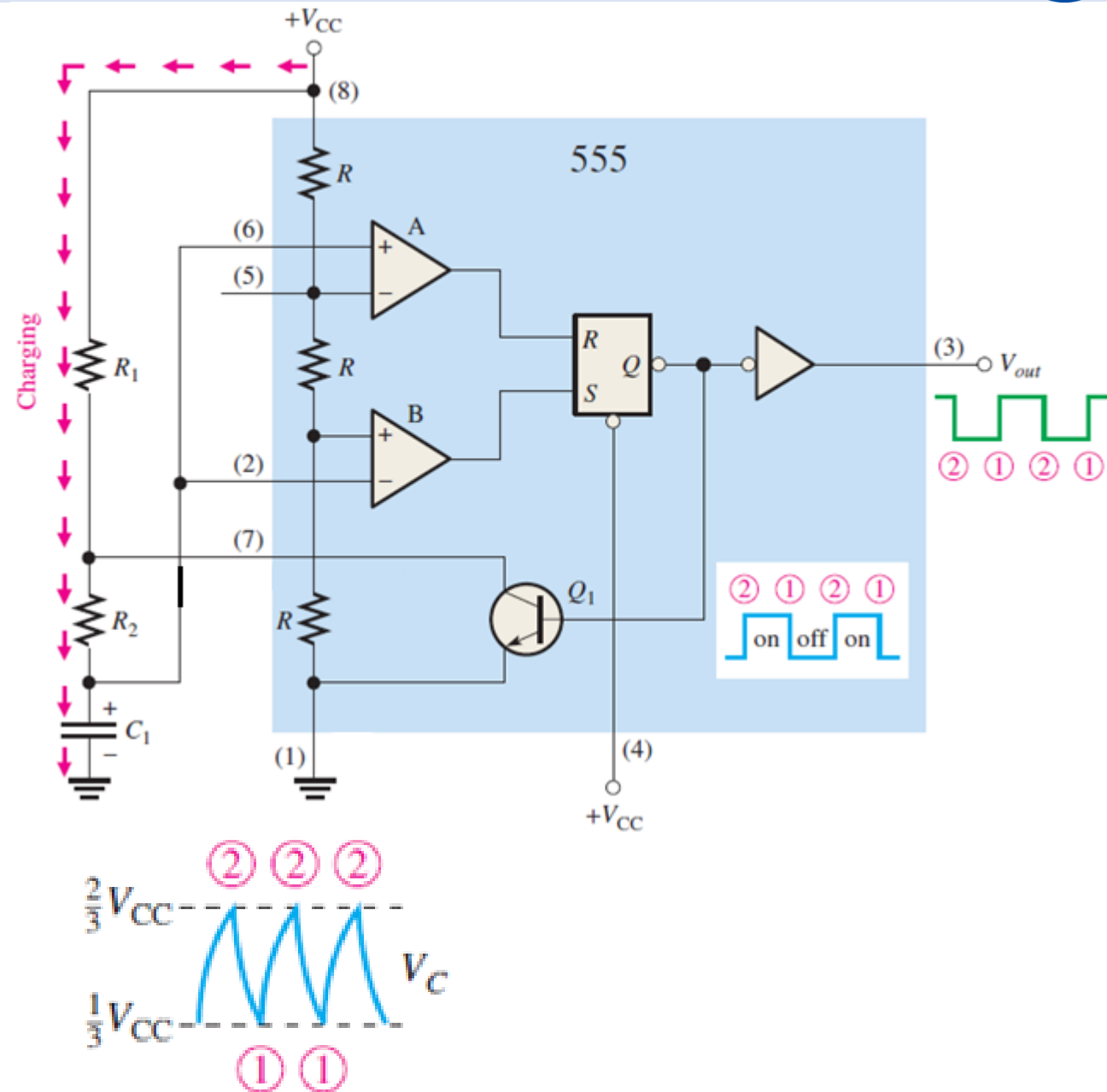
# Astable Mode

- Initially, when the power is just turned on, the capacitor (C1) remain uncharged and thus the trigger (pin 2) and threshold (pin 6) is at 0V. So, output of comparator A is 0 and comparator B is 1. Thus, Q1 is OFF.
- Now, C1 begins charging through R1 and R2, indicated in Figure. When C1 is just below  $\frac{1}{3} V_{CC}$ , the output of comparator B is 1 and the flip-flop is set. Thus, the output (pin3) is 1.
- The transistor Q1 is OFF.
- When C1 charges beyond  $\frac{1}{3} V_{CC}$ , then the output of comparator B is 0. However, the output (pin3) is still 1 and the transistor is still OFF.
- So during the charging phase the output (pin3) of the 555 timer remains HIGH.


 
# Astable Mode

- Once the voltage of the C1 is just beyond  $\frac{2}{3} V_{CC}$ , the output of the comparator A becomes 1.
- This resets the flip-flop. Thus the output (pin3) is 0. However, Q1 turns on and the capacitor starts discharging.
- Once the voltage of C1 is below  $\frac{2}{3} V_{CC}$ , the output of the comparator A becomes 0. However, the capacitor still discharges. And the output (pin 3) remains 0.
- Therefore, during the discharge phase the output of the 555 time is 0.
- When the capacitor C1 discharges just below  $\frac{1}{3} V_{CC}$ , the output of the comparator becomes 1 and the flip-flop is again set.
- Thus, again the charging cycle begins.



# Astable Mode

- The capacitor charges through  $R_1$  and  $R_2$  and during the charging phase the output is HIGH. Thus, time of the HIGH pulse can be calculated as:

$$T_H = 0.693C_1(R_1 + R_2)$$

- The capacitor discharges through only  $R_2$  and during the discharging phase the output is LOW. Thus time of LOW pulse can be calculated as:

$$T_L = 0.693C_1(R_2)$$

- The time period of the oscillator is:


$$T = T_H + T_L = 0.693C_1(R_1 + 2R_2)$$

- Frequency of the oscillator is:

$$F = \frac{1}{0.693C_1(R_1 + 2R_2)}$$

- Duty cycle:

$$D.C. = \frac{T_H}{T_H + T_L}$$

 

# Mathematical Problem

- Design an oscillator for a frequency of 200Hz with a duty cycle of 78%. Determine the time period, high & low time,  $R_2$  and  $R_1$  (assume  $C_1 = 10\mu\text{F}$ )

- Time Period (T):

$$T = \frac{1}{F} = \frac{1}{200\text{Hz}} = 0.005\text{s}$$

- Time HIGH and Time LOW:

$$T_H = .78 \times 0.005\text{s} = 0.0039\text{s} = 3.9\text{ms}$$

$$T_L = .22 \times 0.005\text{s} = 0.0011 = 1.1\text{ms}$$

- Value of  $R_2$ :

$$T_L = 0.693R_2C_1$$

$$1.1\text{ms} = 0.693 \times R_2 \times 10\mu\text{F}$$

$$R_2 = 158.7\Omega$$

- Value of  $R_1$ :

$$3.9\text{ms} = 0.693(R_1 + R_2)C_1$$

$$3.9\text{ms} = 0.693(R_1 + R_2)10\mu\text{F}$$


$$R_1 = 404.1\Omega$$

# Monostable Mode

Monostable Mode Schematic:


The components which determine the operation are:

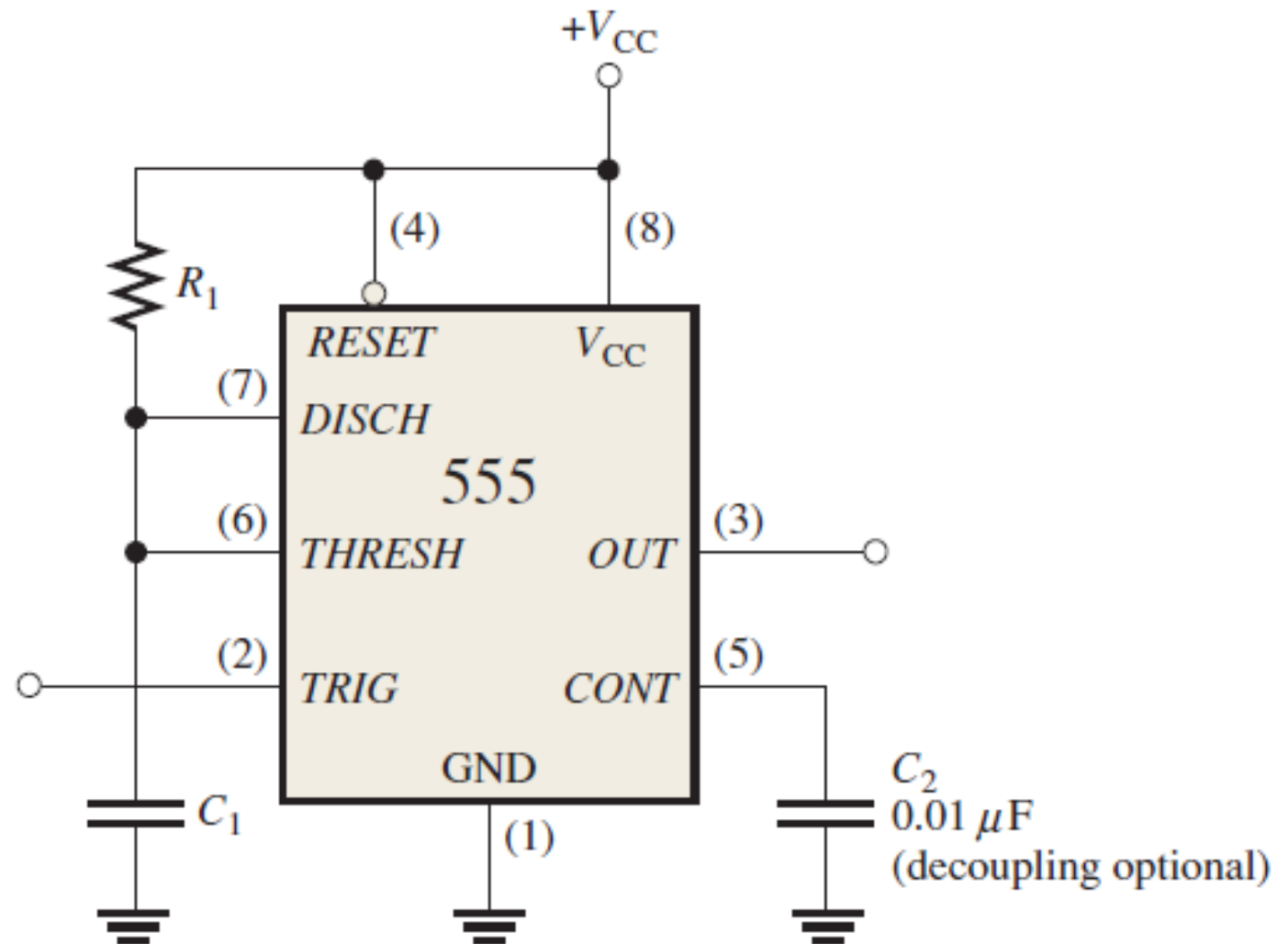- One resistors ( $R_1$ )
- One capacitor ( $C_1$ )


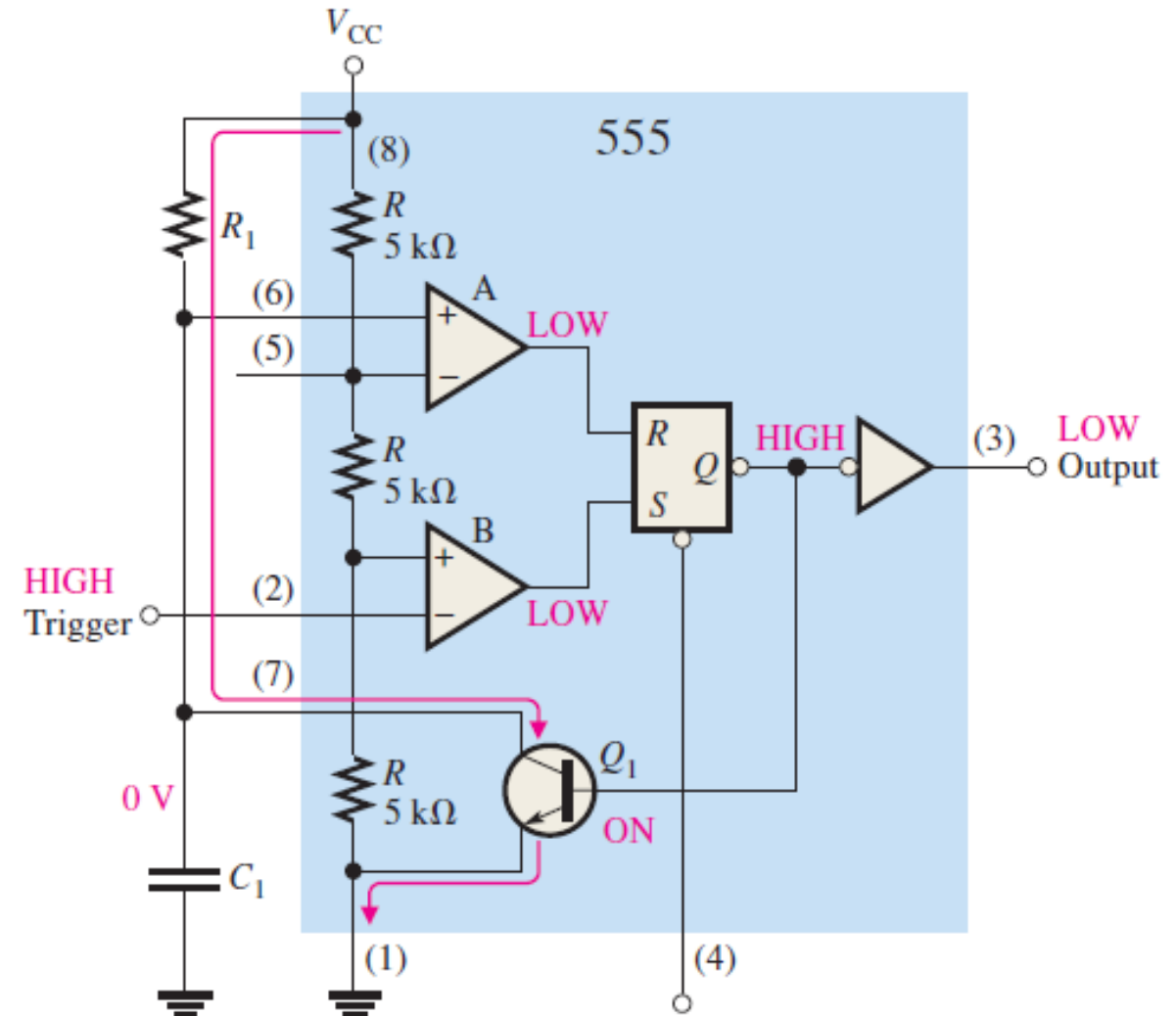
# Monostable Mode


- Prior to triggering the output is LOW and is in the stable state.
- The discharge capacitor Q1 is ON.
- Thus C1 is bypassed and hence C1 do not charge.





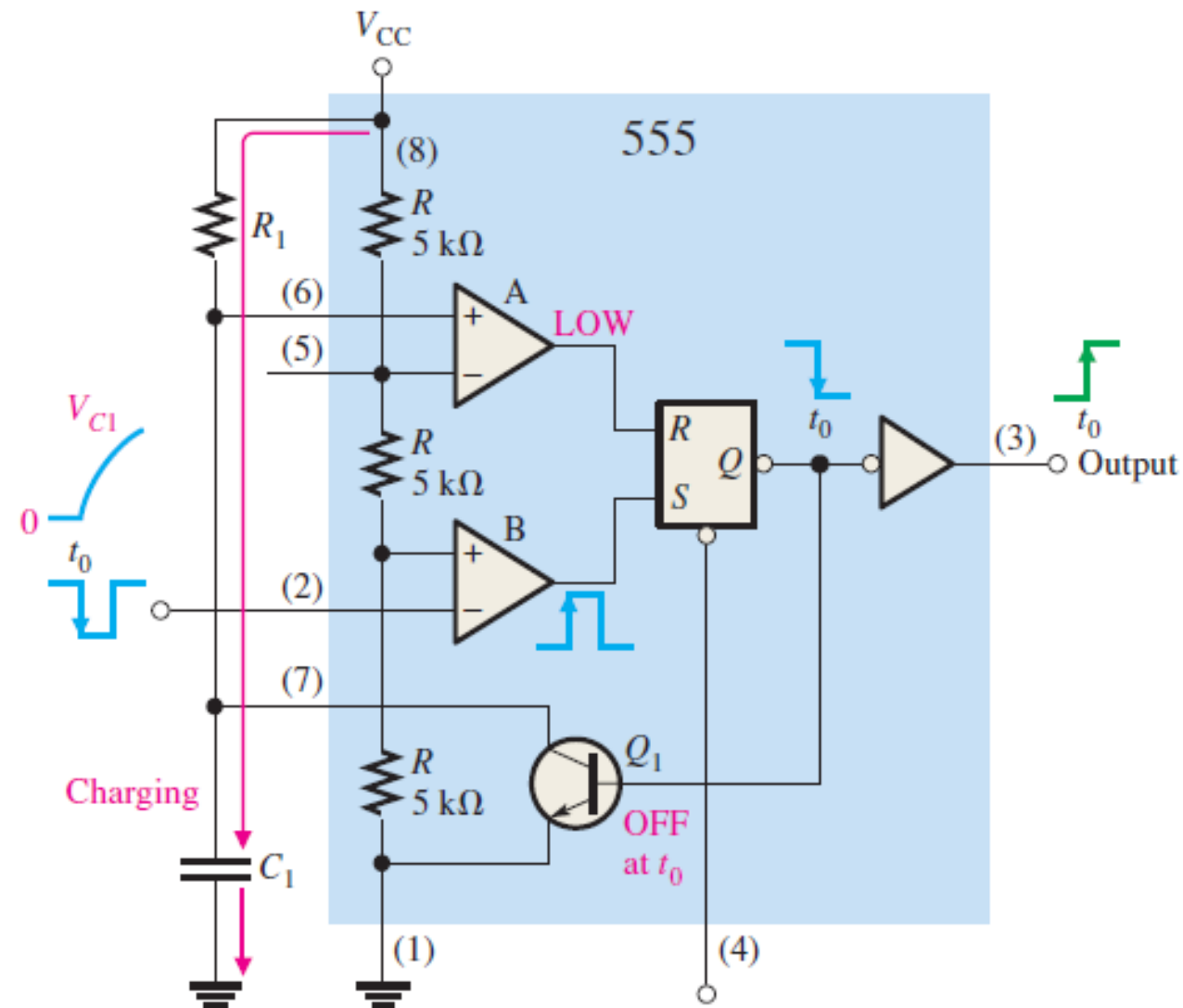
# Monostable Mode

- At time,  $t_0$ , a negative going triggering pulse is applied.
- Hence the trigger pin becomes less than  $1/3 V_{CC}$ . Thus the output of comparator B becomes 1.
- This sets the flip-flop and the output (pin 3) is HIGH.
- Consequently, the transistor Q1 is OFF and the capacitor starts charging through  $R_1$ .
- The capacitor charges till it reaches  $2/3 V_{CC}$ .
- The time required for the capacitor to charge till  $2/3 V_{CC}$  determines the width of the HIGH pulse (unstable state)



- $$T_W = 1.1 R_1 C_1$$

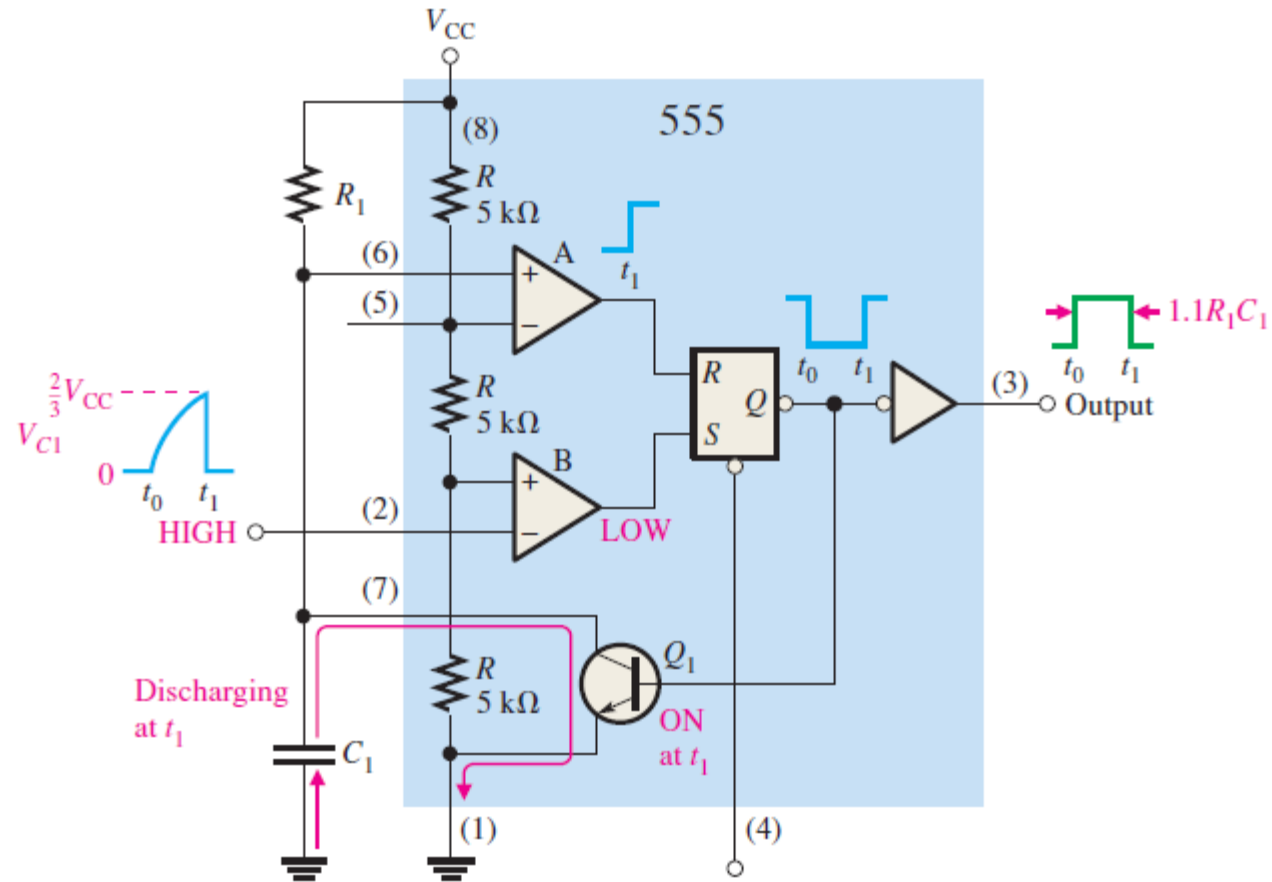

1. Thomas L. Floyd, “Digital Fundamentals” 11<sup>th</sup> edition, Prentice Hall – Pearson Education.

# Thank You